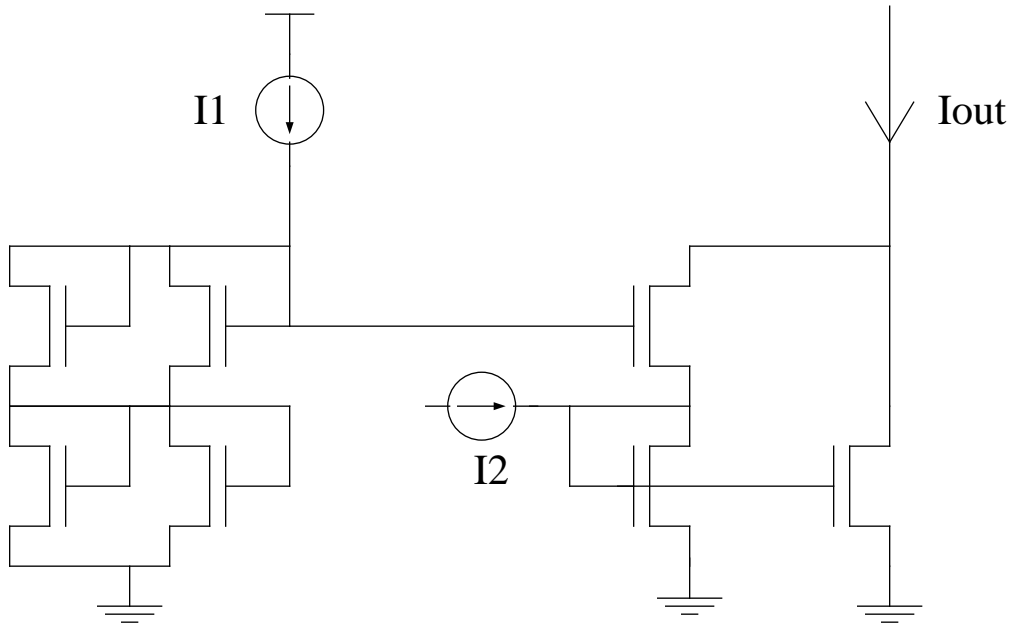


## EEL 6935: HW#2


**Due Wednesday, September 24, 2002 in class. Late homework loses  $e^{\# \text{ of days late}} - 1$  percentage points. See the current late penalty at <http://www.cnel.ufl.edu/hybrid/harris/latepoints.html>**

For the first three problems, solve for  $I_{out}$  as a function of the inputs assuming subthreshold operation. Keep in mind that each circuit computes a very useful function. Assume  $\kappa = 1$  and derive your answer. Show all of your work and explicitly state all assumptions, e.g. which transistors are in saturation, subthreshold operation, matching of devices, etc.


1. Solve for  $I_{out}$  as a function of  $I_1$  and  $I_2$  for the following translinear circuit. Note that  $I_2$  can be positive or negative so make sure to describe the range of values of  $I_2$  where your result is valid.



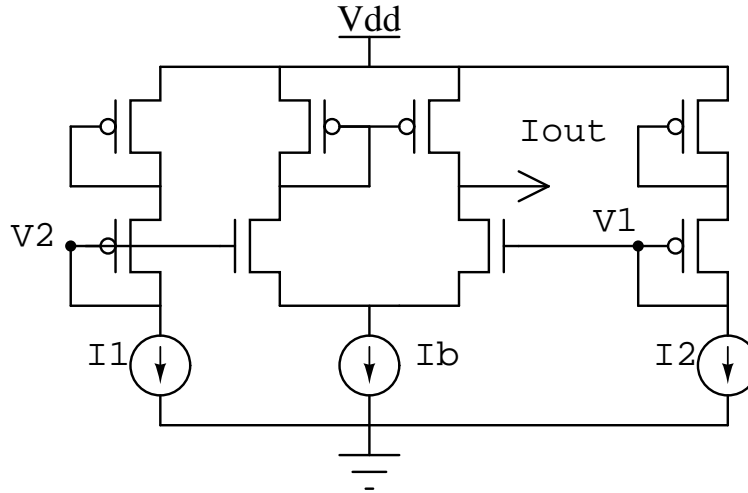2. Solve the following circuit for  $I_{out}$  in terms of  $I_1$ ,  $I_2$ ,  $I_B$ , and any other circuit parameters you feel you might need. Make any reasonable assumptions but clearly state and justify them. Assume that  $\kappa = 1$  for all devices. For full credit, you must simplify as much as possible (hint: there should be no *transcendental functions*<sup>1</sup> in the answer).



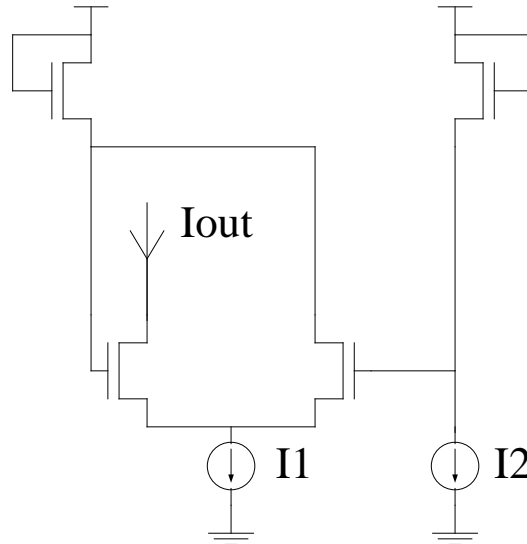3. Solve for  $I_{out}$  as a function of  $I_1$  and  $I_2$ . You will have to think a little bit more about this circuit than those previously worked on.



<sup>1</sup>A function which “transcends,” (i.e., cannot be expressed in terms of) algebra.

For the final questions, you must have access to a circuit simulator. Examples include CADENCE SPECTRE, PSPICE, HSPICE, and winspice but use whichever simulator you feel comfortable with. Note that winspice is shareware that is available from [www.winspice.com](http://www.winspice.com). We will be using the 0.6um AMI process available through MOSIS. Complete information about the process is available through

<http://www.mosis.org/Technical/Processes/proc-ami-c5n.html>

UF CADENCE users will already have this process available but other simulators may require the following model files available at

<http://www.cnel.ufl.edu/hybrid/courses/EEL6935/nmos.txt>

and

<http://www.cnel.ufl.edu/hybrid/courses/EEL6935/pmos.txt>

4. For a 6um x 6um nfet transistor, plot the  $I_{ds}$  vs.  $V_{gs}$  curve for the device. Scan  $V_{gs}$  from 0 to  $V_{dd}$ . Calculate the approximate value of  $\kappa$  below threshold. Completely describe how you performed the calculation. Also, come up with a rule for defining what the threshold of the transistor is.
5. For a 6um x 6um nfet transistor, plot the  $I_{ds}$  vs.  $V_{ds}$  curve for the device for several below threshold values of  $V_{gs}$ . Calculate the approximate value of the Early Voltage  $V_E$ . Completely describe how you performed the calculation. Also, come up with a rule for defining what the saturation voltage is.
6. Verify your solution of Problem 3 for  $I_{out}$  as a function of  $I_1$  and  $I_2$ . Show plots and compare your theoretical solution to your simulation results.